



# General License Class

## Chapter 4 Components & Circuits (Part 2)



## Active Components

- Semiconductor Components
  - Semiconductors are materials that do not conduct as well as metals, but better than insulators.
    - Can modify properties by adding controlled amounts of other materials called “dopants”.
- Atomic Structure
  - Nucleus (Protons & Neutrons)
  - Electrons
    - Orbits (Shells)
    - 8 electrons completes a shell




# Active Components

- Semiconductor Components

- 4 electrons in outer shell.

- Silicon.
- Germanium.

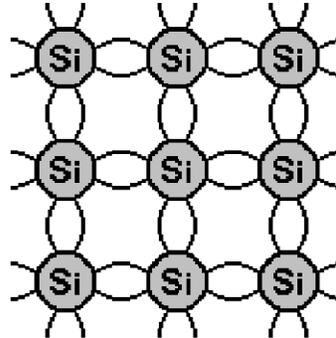


# Active Components

- Semiconductor Components

- "N" Material

- Add element with 5 electrons in outer shell (donor Impurity).

- Arsenic.
- Antimony.
- Phosphorus.

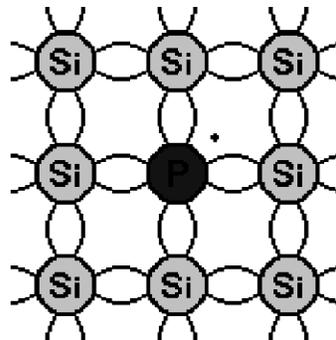




# Active Components

- Semiconductor Components

- "P" Material

- Add element with 3 electrons in outer shell (acceptor Impurity).

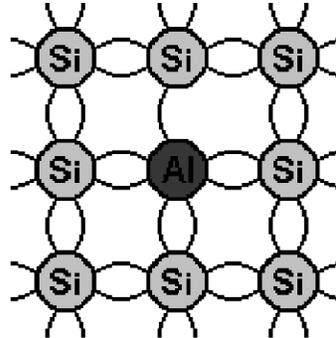- Aluminum.
      - Gallium.
      - Indium.



# Active Components

- Semiconductor Components

- Majority Charge Carrier

- N-Type Material = Electron
    - P-Type Material = Hole

- Other semiconductor materials

- Gallium-Arsenide (GaAs)
      - LED's
      - Microwave frequencies.
    - Gallium-Arsenide-Phosphide (GaAsP)
      - LED's




# Active Components

- Semiconductor Components

- Diodes & Rectifiers

- Junction diodes.

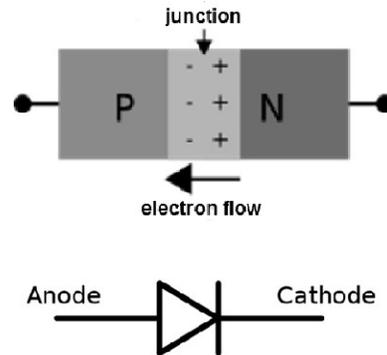- A P-N junction blocks current flow in one direction & allows current to flow in the other direction.





# Active Components

- Semiconductor Components

- Diodes & Rectifiers

- Junction diodes.

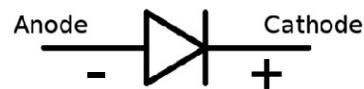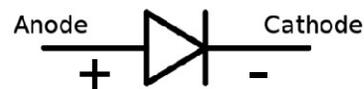- Voltage applied in the forward direction is called "forward bias".
        - Large current flow.
      - Voltage applied in the reverse direction is called "reverse bias".
        - Minimal current flow.





# Active Components

- Semiconductor Components
  - Diodes & Rectifiers
    - Diodes designed for low-power signals are called “signal” or “switching” diodes.
    - Diodes designed for high power circuits are called “rectifiers”.
      - Maximum reverse voltage as high as 1000 Volts.
      - Maximum forward current as high as 200 Amp.




# Active Components

- Semiconductor Components
  - Diodes & Rectifiers
    - Diode Ratings
      - Peak Inverse Voltage (PIV).
        - Maximum voltage in reverse direction (reverse bias).
      - Maximum Average Forward Current.
        - Maximum Allowable Junction Temperature.
      - Forward Voltage Drop.
        - Silicon = 0.7 Volts (approx.)
        - Germanium = 0.3 Volts (approx.)
        - GaAs & GaAsP = 1.2 Volts to 1.5 Volts (approx.)


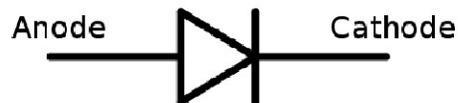
# Active Components

- Semiconductor Components
  - Diodes & Rectifiers
    - Diode Types
      - PIN diode.
        - Low forward voltage drop.
        - RF switching & control.



# Active Components

- Semiconductor Components
  - Diodes & Rectifiers
    - Diode Types
      - Schottky Diode.
        - Low junction capacitance allows operation at VHF & UHF.
        - Lower forward voltage drop.
          - Power supply rectifiers.






# Active Components

- Semiconductor Components
  - Diodes & Rectifiers
    - Diode Types
      - Varactor Diodes (VariCap).
        - Operates with reverse bias.
        - Varying voltage varies junction capacitance.
        - Used for variable-frequency oscillators & for FM modulators.


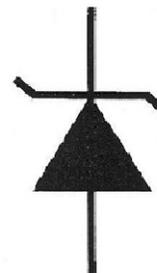
# Active Components

- Semiconductor Components
  - Diodes & Rectifiers
    - Diode Types
      - Zener diode.
        - Operates with reverse bias.
        - Operates at avalanche (breakdown) voltage.
        - Designed to withstand avalanche current with proper heat sink.
        - Large change in avalanche current results in small change in voltage.





# Active Components

- Semiconductor Components
  - Bipolar & Field-Effect Transistors
    - Adding another layer to a diode creates a device capable of amplifying a signal.
      - 1<sup>st</sup> Transistor was created at Bell Labs in late 1947.



# Active Components

- Semiconductor Components
  - Bipolar Transistors
    - Changing the amount of current (small) flowing through the base-emitter junction controls the amount of current (large) flowing from the collector to the emitter.
    - Bipolar transistors exhibit current gain.
      - $\beta = I_C / I_B$
      - $\alpha = I_C / I_E$




# Active Components

- Semiconductor Components
  - Bipolar Transistors


## Bipolar Transistor Circuit Symbols

NPN Transistor

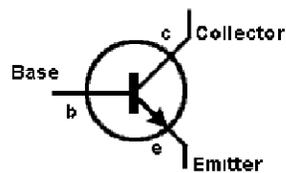

**N** Never  
**P** Points  
**N** iN

PNP Transistor

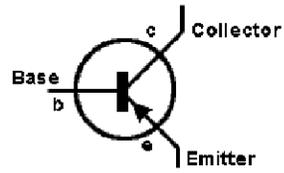


**P** Points  
**N** iN  
**P** Permanently


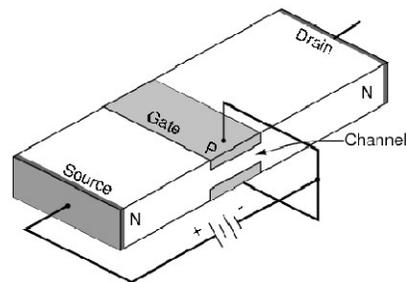
# Active Components


- Semiconductor Components
  - Field-Effect Transistors (FET)
    - Gate voltage controls channel current.
    - Gain measured in Transconductance
      - Siemens
    - High input impedance.
    - Enhancement Mode
    - Depletion Mode





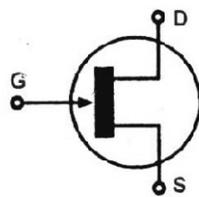
# Active Components

- Semiconductor Components
  - Field-Effect Transistors
    - Junction Field-Effect Transistor (JFET)



*N-Channel JFET*

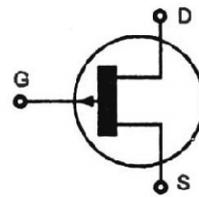


*P-Channel JFET*




# Active Components

- Semiconductor Components
  - Field-Effect Transistors
    - Metal Oxide Semiconductor Field-Effect Transistor (MOSFET)

NMOS Transistor  
(n-channel MOSFET)

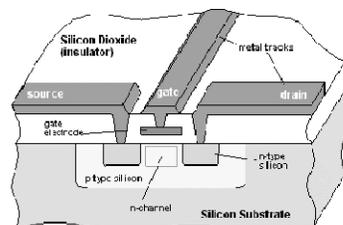


PMOS Transistor  
(p-channel MOSFET)

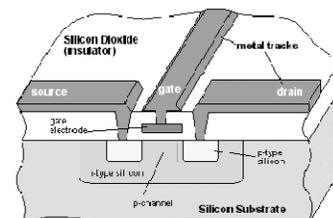


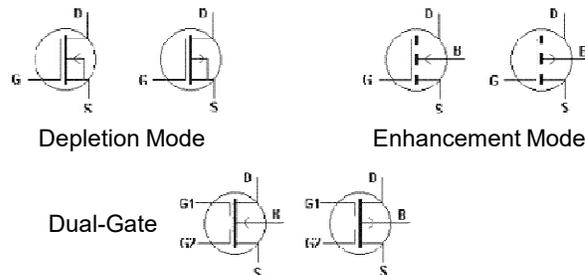
# Active Components

- Semiconductor Components
  - Field-Effect Transistors
    - Metal Oxide Semiconductor Field-Effect Transistor (MOSFET)



# Active Components


- Semiconductor Components
  - Bipolar & Field-Effect Transistors
    - High gain makes both bipolar transistors & FET's useful as switches.
      - Low base current or low gate voltage\* puts transistor into "cutoff" -- little or no current flow.
        - Additional reduction of base current or gate voltage does not result in any further reduction in current flow.
      - High base current or high gate voltage\* puts transistor into "saturation" – maximum current flow.
        - Additional increase of base current or gate voltage does not result in any further increase in current flow.

\*Assuming enhancement-mode FET.


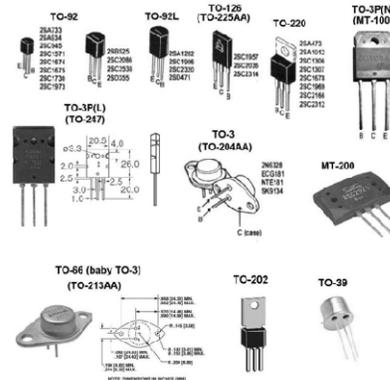
# Active Components

- Semiconductor Components
  - Bipolar & Field-Effect Transistors
    - Transistors come in wide variety of packages.
    - Some high-power cases have collector or source directly connected to case.
      - Better heat transfer.
    - **Must be insulated from heat sink or chassis.**



# Active Components


- Vacuum Tubes
  - Oldest amplification device.
    - Invented by Lee De Forest in 1906.





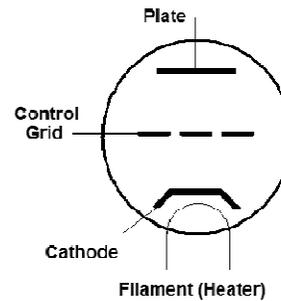
# Active Components

- Vacuum Tubes
  - Triode
    - Simplest tube capable of amplification.
    - 3 Elements
      - Cathode.
      - Control Grid (Grid).
      - Plate (Anode).


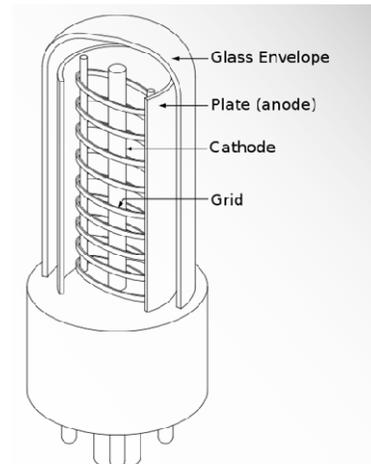
# Active Components


- Vacuum Tubes
  - Cathode.
    - Source of electrons.
      - Directly heated.
      - Indirectly heated.
    - At or near ground potential.
    - High current.





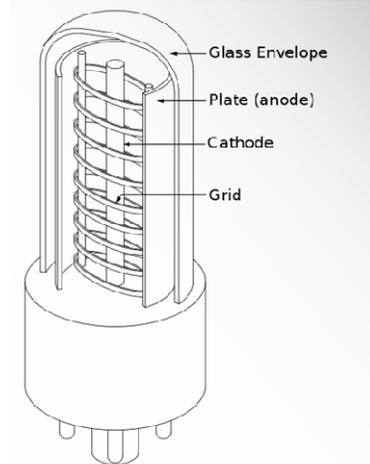
# Active Components

- Vacuum Tubes
  - Control Grid (Grid).
    - Fine wire mesh.
    - Controls flow of electrons from cathode to plate.
    - Small negative voltage.
      - Tens of volts.
    - Low current.


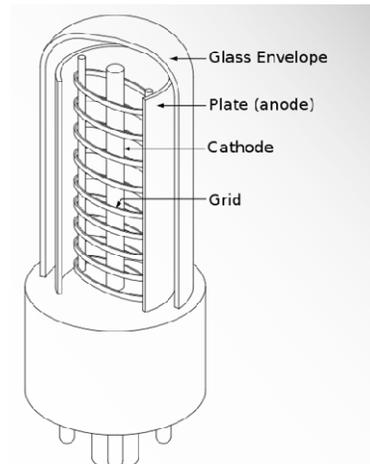
# Active Components


- Vacuum Tubes
  - Plate (Anode).
    - Collects electrons emitted by cathode.
    - High positive voltage.
      - Hundreds or thousands of volts.
    - High current.





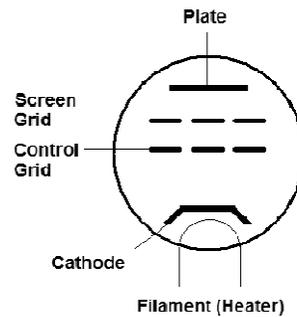
# Active Components

- Vacuum Tubes
  - Tetrode
    - 4 Elements
      - Cathode.
      - Control Grid.
      - Screen Grid.
      - Plate .


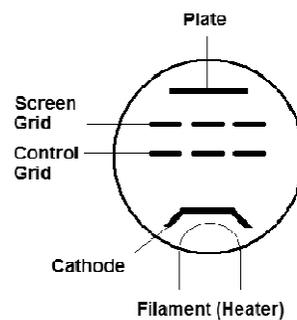
# Active Components


- Vacuum Tubes
  - Tetrode
    - Screen Grid.
      - Reduces capacitance between plate & control grid, preventing self-oscillation.
      - Medium positive voltage.
        - 150-200 Volts.
      - Low Current.





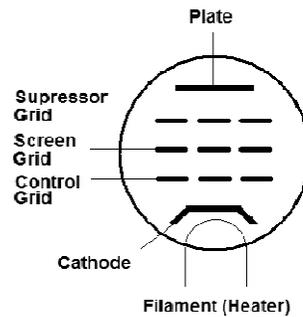
# Active Components

- Vacuum Tubes
  - Pentode
    - 5 Elements
      - Cathode.
      - Control Grid.
      - Screen Grid.
      - Suppressor Grid.
      - Plate .


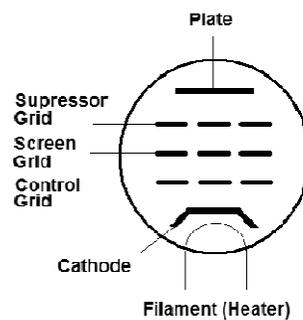
# Active Components

- Vacuum Tubes
  - Pentode
    - Suppressor Grid.
      - Reduces “splashback” of electrons from plate to screen grid.
      - At or near cathode potential.
        - Often directly connected to cathode.
      - Low current.





## Active Components

- Vacuum Tubes



## Active Components

- Analog & Digital Integrated Circuits
  - Many transistors, diodes, & interconnections can be made on a single silicon wafer almost as easily as a single transistor. The result is called an integrated circuit.




# Active Components

- Analog & Digital Integrated Circuits
  - Analog integrated circuits.
    - Used for amplification, filtering, voltage regulation, and many other applications.
      - Operational Amplifier.
      - Linear Voltage Regulator.


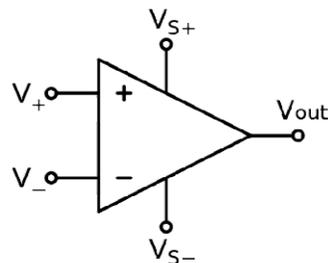
# Active Components


- Analog & Digital Integrated Circuits
  - Analog integrated circuits.
    - Operational Amplifier.
      - Circuit characteristics totally controlled by external components.
      - Amplifiers.
      - Active filters.
      - Adding signals.




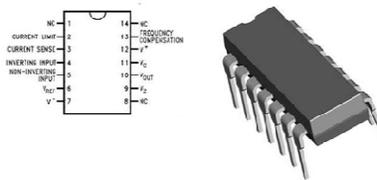
# Active Components

- Analog & Digital Integrated Circuits
  - Analog integrated circuits.
    - Linear Voltage Regulators.
      - LM-723.
        - External Components required.



# Active Components

- Analog & Digital Integrated Circuits
  - Analog integrated circuits.
    - Linear Voltage Regulators.
      - IC 3-Terminal Regulators.
        - Thermal shutdown.
        - Overvoltage protection.
        - Foldback current limiting.
        - LM78Lxx -- 100 mA.
        - LM78xx -- 1 Amp.
        - LM78Hxx -- 3 Amps.






# Active Components

- Analog & Digital Integrated Circuits
  - Digital integrated circuits.
    - Binary (base2) number system used for digital processing.
      - Only digits 0 & 1 are used.
      - Any number can be represented by a string of 0's & 1's.
        - 0 = 000, 1 = 001, 2 = 010, 3 = 011, 4 = 100, etc.
      - "0" & "1" can be easily represented by the "off" & "on" states of a transistor or similar device.


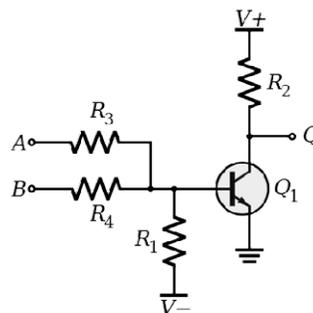
# Active Components


- Analog & Digital Integrated Circuits
  - Digital integrated circuits.
    - Logic Families.
      - Resistor-Transistor-Logic (RTL).
        - 1<sup>st</sup> digital logic family (1961).
        - High power consumption.
        - No longer used.
          - Replaced by DTL.





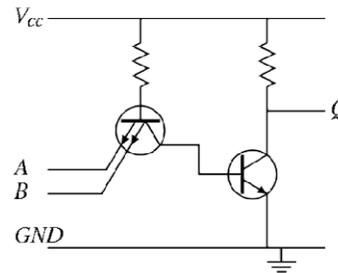
# Active Components

- Analog & Digital Integrated Circuits
  - Digital integrated circuits.
    - Logic Families.
      - Transistor-Transistor-Logic (TTL).
        - Replaced RTL & DTL.
        - +5V supply voltage.
        - Low noise immunity.


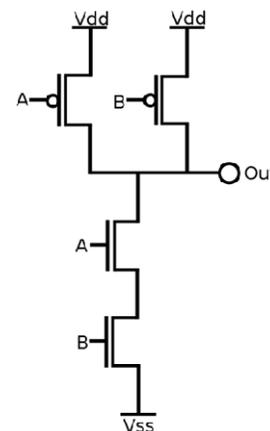
# Active Components


- Analog & Digital Integrated Circuits
  - Digital integrated circuits.
    - Logic Families.
      - Complimentary Metal-Oxide Semiconductor (CMOS).
        - Replacing TTL.
        - +5V - 15V supply voltage.
        - High noise immunity.




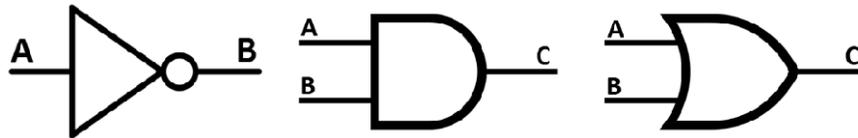
# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - Basic building block of a digital circuit is called a “gate”.
      - NOT (inverting) gate.
      - AND gate.
      - OR gate.



# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - One-input elements.
      - Non-inverting buffer.
      - Inverting buffer or “Not” gate.





# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - AND gate.
      - Output true only if ALL inputs are true
    - NAND (Not-AND) gate.
      - Output false only if ALL inputs are true.



A	B	C
0	0	0
0	1	0
1	0	0
1	1	1



A	B	C
0	0	1
1	0	1
0	1	1
1	1	0



# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - OR gate.
      - Output true if one or more of the inputs are true.
    - NOR (Not-OR) gate.
      - Output false if one or more of the inputs are true.



A	B	C
0	0	0
0	1	1
1	0	1
1	1	1



A	B	C
0	0	1
1	0	0
0	1	0
1	1	0



# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - XOR (Exclusive-OR) gate.
      - Output true if one and only one of the inputs is true.
    - XNOR (Exclusive-NOR) gate.
      - Output false if one and only one of the inputs is true.



A	B	C
0	0	0
0	1	1
1	0	1
1	1	0



A	B	C
0	0	1
1	0	0
0	1	0
1	1	1



# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - Sequential logic
      - Current state dependent on both current inputs and previous state.
      - Must include some form of "memory".




# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - Flip-flop
      - a.k.a -- Bi-stable multivibrator, latch.
      - Several different types.
        - S-R, J-K, D, T.
        - Gated, non-gated.
        - Clocked, non-clocked.
      - Can be used as frequency divider.
      - Can be used as frequency counter.



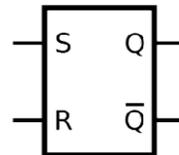
# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - Set-Reset (SR) Latch
      - Most basic latch type.



S	R	Action
0	0	No change
0	1	Q = 0
1	0	Q = 1
1	1	Forbidden

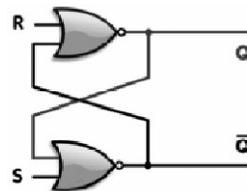




# Active Components



- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - J-K flip-flop
      - Adds toggle function to SR latch.
      - Must be clocked.

Clock (>)	J	K	Action
0	--	--	No change
1	0	0	No change
1	0	1	Q = 0
1	1	0	Q = 1
1	1	1	Toggle (Q = not Q)

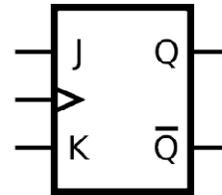
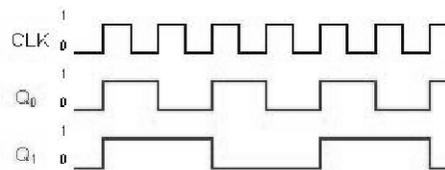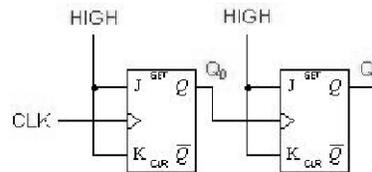
# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - Frequency divider.






# Active Components


- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - D flip-flop
      - Most common type.
      - Computer RAM.
      - Must be clocked.

Clock (>)	D	Action
0	--	No change
1	0	Q = 0
1	1	Q = 1

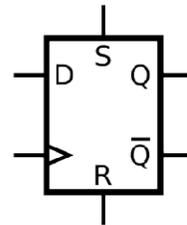
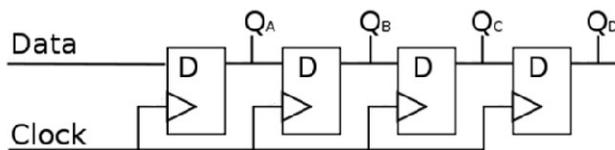
# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - Shift Register
      - Cascaded D flip-flops.
      - Shifts data from stage to stage.
      - Converts serial data to parallel data.
      - Converts parallel data to serial data.






# Active Components


- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - T flip-flop
      - Toggles state with each clock pulse.
      - D flip-flop with Q output connected to D input.

Clock (>)	T	Action
0	--	No change
1	0	No change
1	1	Toggle (Q = not Q)

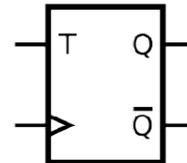
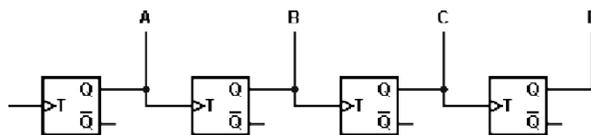
# Active Components

- Analog & Digital Integrated Circuits
  - Digital Logic Basics.
    - Digital Counter
      - Cascaded T flip-flops.
      - Counts number of input pulses.
      - Number of states =  $2^N$  where N = number of stages.
        - For example: 3-stage counter has 8 states.






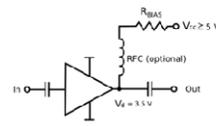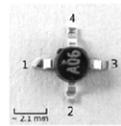
# Active Components

- RF Integrated Circuits.
  - Monolithic Microwave Integrated Circuit (MMIC)
    - VHF, UHF, microwaves.
    - Typically  $50\Omega$
    - Low Noise Figure
      - 3.5 dB to 6.0 dB
    - Microstrip construction

Cascadable Monolithic Microwave Integrated Circuit (MMIC)  
MSA-0685




- 1- Input
- 2 - Ground (GND)
- 3 - Output
- 4 - Ground (GND)

3 dB Bandwidth: DC up to 0.8 GHz  
Gain: typical 18.5 dB at 0.5 GHz


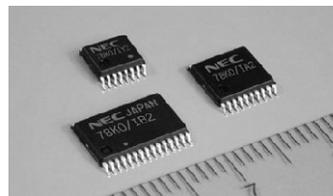
# Active Components


- Microprocessors & Related Components.
  - Microprocessor.
    - A computer on a chip.
      - Thousands of gates.
      - Tens of thousands of transistors & diodes.
  - Microcontroller.
    - Microprocessor with added interfaces to input & output devices.





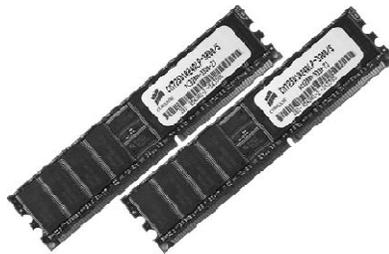
# Active Components

- Microprocessors & Related Components.
  - Memory
    - Volatile
      - Data is lost when power is off.
      - Random Access Memory (RAM)


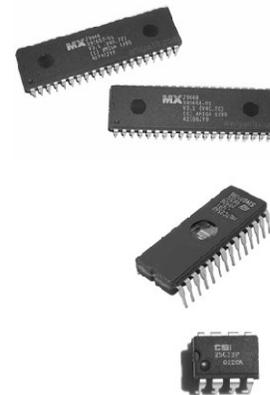
# Active Components

- Microprocessors & Related Components.
  - Memory
    - Non-Volatile
      - Data is retained when power is off.
      - Read-Only Memory (ROM)
      - Programmable Read-Only Memory (PROM)
      - Erasable Programmable Read-Only Memory (EPROM)
      - Electrically Erasable Programmable Read-Only Memory (EEPROM)





# Active Components

- Microprocessors & Related Components.
  - Interfaces.
    - Serial
      - One bit transferred at a time.
    - Parallel
      - Multiple bits transferred at a time.



# Active Components

- Microprocessors & Related Components.
  - Interfaces.
    - Serial
      - One bit transferred at a time.
      - RS-232 (COM ports).
        - Commonly used to connect amateur transceivers to personal computers.
      - Universal Serial Bus (USB).
        - Replacing RS-232.
        - Commonly used to connect amateur transceivers to personal computers.
    - Ethernet.



# Active Components

- Microprocessors & Related Components.
  - Interfaces.
    - Parallel
      - Multiple bits transferred at a time.
      - Used for connections to mass storage devices.
        - Integrated Drive Electronics (IDE)
        - Small Computer System Interface (SCSI)
      - Centronics® Parallel Printer Port.
      - Being replaced by high-speed serial interfaces.



# Active Components

- Visual Interfaces.
  - Indicator
    - Displays on/off state of a single item.
    - Incandescent Lamp
      - Largely replaced by LED's.
    - Light-Emitting-Diode (LED)
      - Emits light when forward biased.
      - Faster than incandescent lamp.
      - Less power than incandescent lamp.
      - Less heat than incandescent lamp.
      - Longer life than incandescent lamp.






# Active Components

- Visual Interfaces.
  - Display
    - Displays text or graphical information.
    - Most common type in amateur equipment is the liquid crystal display (LCD).
      - Requires illumination.
        - Ambient light.
        - Back light.


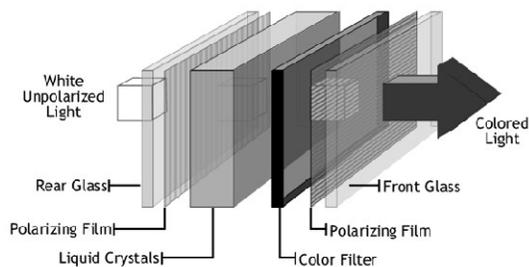
# Active Components

- Visual Interfaces.
  - Liquid-Crystal Displays
    - Rotates polarization of light passing through it.
    - Applying voltage across crystal changes polarization.





**G6A03 -- What is the approximate junction threshold voltage of a germanium diode?**

- A. 0.1 volt
- ➔ B. 0.3 volts
- C. 0.7 volts
- D. 1.0 volts



**G6A05 -- What is the approximate junction threshold voltage of a conventional silicon diode?**

- A. 0.1 volt
- B. 0.3 volts
- ➔ C. 0.7 volts
- D. 1.0 volts



**G6A06 -- Which of the following is an advantage of using a Schottky diode in an RF switching circuit rather than a standard silicon diode?**

- A. Lower capacitance
- B. Lower inductance
- C. Longer switching times
- D. Higher breakdown voltage



**G6A07 -- What are the stable operating points for a bipolar transistor used as a switch in a logic circuit?**

- A. Its saturation and cutoff regions
- B. Its active region (between the cutoff and saturation regions)
- C. Its peak and valley current points
- D. Its enhancement and depletion modes



**G6A08 -- Why must the cases of some large power transistors be insulated from ground?**

- A. To increase the beta of the transistor
- B. To improve the power dissipation capability
- C. To reduce stray capacitance
- ➔ D. To avoid shorting the collector or drain voltage to ground



**G6A09 -- Which of the following describes the construction of a MOSFET?**

- A. The gate is formed by a back-biased junction
- ➔ B. The gate is separated from the channel with a thin insulating layer
- C. The source is separated from the drain by a thin insulating layer
- D. The source is formed by depositing metal on silicon



**G6A10 -- Which element of a triode vacuum tube is used to regulate the flow of electrons between cathode and plate?**

- ➔ A. Control grid
- B. Heater
- C. Screen grid
- D. Trigger electrode



**G6A11 -- Which of the following solid state devices is most like a vacuum tube in its general operating characteristics?**

- A. A bipolar transistor
- ➔ B. A field effect transistor
- C. A tunnel diode
- D. A varistor



**G6A12 -- What is the primary purpose of a screen grid in a vacuum tube?**

- A. To reduce grid-to-plate capacitance
- B. To increase efficiency
- C. To increase the control grid resistance
- D. To decrease plate resistance



**G6B01 -- Which of the following is an analog integrated circuit?**

- A. NAND Gate
- B. Microprocessor
- C. Frequency Counter
- D. Linear voltage regulator



**G6B02 -- What is meant by the term MMIC?**

- A. Multi Megabyte Integrated Circuit
- ➔ B. Monolithic Microwave Integrated Circuit
- C. Military Manufactured Integrated Circuit
- D. Mode Modulated Integrated Circuit



**G6B03 -- Which of the following is an advantage of CMOS integrated circuits compared to TTL integrated circuits?**

- ➔ A. Low power consumption
- B. High power handling capability
- C. Better suited for RF amplification
- D. Better suited for power supply regulation



**G6B04 -- What is meant by the term ROM?**

- A. Resistor Operated Memory
- ➔ B. Read Only Memory
- C. Random Operational Memory
- D. Resistant to Overload Memory



**G6B05 -- What is meant when memory is characterized as non-volatile?**

- A. It is resistant to radiation damage
- B. It is resistant to high temperatures
- ➔ C. The stored information is maintained even if power is removed
- D. The stored information cannot be changed once written



**G6B06 -- What kind of device is an integrated circuit operational amplifier?**

- A. Digital
- B. MMIC
- C. Programmable Logic
- D. Analog



**G6B07 -- Which of the following is an advantage of an LED indicator compared to an incandescent indicator?**

- A. Lower power consumption
- B. Faster response time
- C. Longer life
- D. All of these choices are correct



**G6B08 -- How is an LED biased when emitting light?**

- A. Beyond cutoff
- B. At the Zener voltage
- C. Reverse Biased
- D. Forward Biased



**G6B09 -- Which of the following is a characteristic of a liquid crystal display?**

- A. It requires ambient or back lighting
- B. It offers a wide dynamic range
- C. It has a wide viewing angle
- D. All of these choices are correct



**G6B10 -- What two devices in an Amateur Radio station might be connected using a USB interface?**

- A. Computer and transceiver
- B. Microphone and transceiver
- C. Amplifier and antenna
- D. Power supply and amplifier



**G6B11 -- What is a microprocessor?**

- A. A low power analog signal processor used as a microwave detector
- B. A computer on a single integrated circuit
- C. A microwave detector, amplifier, and local oscillator on a single integrated circuit
- D. A low voltage amplifier used in a microwave transmitter modulator stage



**G7B01 -- Complex digital circuitry can often be replaced by what type of integrated circuit?**

- ➔ A. Microcontroller
- B. Charge-coupled device
- C. Phase detector
- D. Window comparator



**G7B02 -- Which of the following is an advantage of using the binary system when processing digital signals?**

- ➔ A. Binary "ones" and "zeros" are easy to represent with an "on" or "off" state
- B. The binary number system is most accurate
- C. Binary numbers are more compatible with analog circuitry
- D. All of these choices are correct



**G7B03 -- Which of the following describes the function of a two input AND gate?**

- A. Output is high when either or both inputs are low
- ➔ B. Output is high only when both inputs are high
- C. Output is low when either or both inputs are high
- D. Output is low only when both inputs are high



**G7B04 -- Which of the following describes the function of a two input NOR gate?**

- A. Output is high when either or both inputs are low
- B. Output is high only when both inputs are high
- ➔ C. Output is low when either or both inputs are high
- D. Output is low only when both inputs are high



**G7B05 -- How many states does a 3-bit binary counter have?**

- A. 3
- B. 6
- C. 8
- D. 16



**G7B06 -- What is a shift register?**

- A. A clocked array of circuits that passes data in steps along the array
- B. An array of operational amplifiers used for tri state arithmetic operations
- C. A digital mixer
- D. An analog mixer



# Break





# Practical Circuits

- Rectifiers & Power Supplies

- Rectifier Circuits.

- Half-Wave Rectifier.

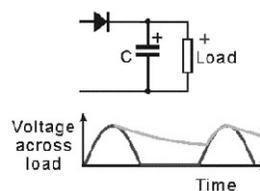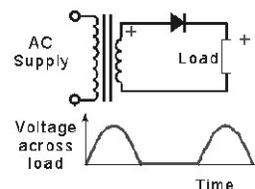- Only one-half of the cycle (180°) delivers power to the load.
      - Creates a series of widely-spaced pulses at the frequency of the input voltage.
      - Very difficult to filter.
      - $V_{Avg} = 0.45 \times V_{AC}$
      - Diode PIV  $\geq 2 \times V_p$
      - Diode  $I_{Max} \geq I_{Load}$






# Practical Circuits

- Rectifiers & Power Supplies

- Rectifier Circuits.

- Full-Wave Rectifier.

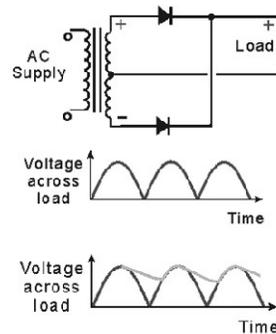- All of the cycle (360°) is used to deliver power to the load.
- Creates a series of closely-spaced pulses at twice the frequency of the input voltage.
- Easier to filter.
- $V_{Avg} = 0.9 \times V_{AC}$
- Diode PIV  $\geq 2 \times V_p$
- Diode  $I_{Max} \geq 0.5 \times I_{Load}$




# Practical Circuits

- Rectifiers & Power Supplies

- Rectifier Circuits.

- Full-Wave Bridge Rectifier.

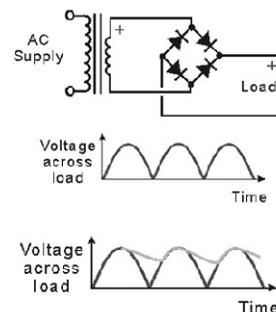- All of the cycle (360°) is used to deliver power to the load.
- Creates a series of closely-spaced pulses at twice the frequency of the input voltage.
- Easier to filter.
- $V_{Avg} = 0.9 \times V_{AC}$
- Diode PIV  $\geq V_p$
- Diode  $I_{Max} \geq 0.5 \times I_{Load}$





# Practical Circuits

- Rectifiers & Power Supplies
  - Rectifier Circuits.

Type of Circuit	Diode PIV Rating	Diode Current Rating
Half-Wave Rectifier	$\geq 2 \times V_p$	$\geq I_{Load}$
Full-Wave Center-Tapped	$\geq 2 \times V_p$	$\geq 0.5 \times I_{Load}$
Full-Wave Bridge	$\geq V_p$	$\geq 0.5 \times I_{Load}$



# Practical Circuits

- Rectifiers & Power Supplies
  - Rectifier Circuits.
    - Diodes in parallel.
      - Diodes can be connected in parallel to increase current capacity, **ONLY** if you put a small-value resistor in series with each diode to equalize the currents between each diode.
    - Diodes in series.
      - Diodes can be connected in series to increase voltage capacity, **ONLY** if you put a large-value resistor in parallel with each diode to equalize the voltage across each diode.




# Practical Circuits

- Rectifiers & Power Supplies
  - Raw output from rectifier is a series of pulses unsuitable for operating electronic equipment.
  - Need filter after rectifier to smooth pulses into a steady DC voltage.
    - Low-pass filter with cut-off frequency well below frequency of pulses.
      - Half-wave rectifier → 60 Hz pulses.
      - Full-wave rectifier → 120 Hz pulses.


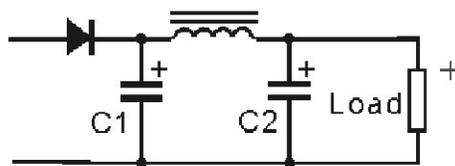
# Practical Circuits

- Rectifiers & Power Supplies
  - Filter Circuits.
    - R-C or L-C network after rectifier to reduce variations in the DC output voltage.
      - Variations are called “ripple”.
      - $\text{Ripple} = 100 \times V_{AC(P-P)} / V_{DC}$





# Practical Circuits

- Rectifiers & Power Supplies
  - Filter Circuits.
    - Choosing the capacitors.
      - Large capacitance.
      - Low effective series resistance (ESR).
      - Computer-grade aluminum electrolytic.
        - Large capacitances & low ESR in smaller case sizes.



# Practical Circuits

- Rectifiers & Power Supplies
  - Filter Circuits.
    - Choosing the inductor.
      - Large inductance.
      - Low series resistance.
      - Not always used.
        - Capacitor may provide sufficient filtering, especially if load is a voltage regulator.





# Practical Circuits

- Rectifiers & Power Supplies
  - Power Supply Safety.
    - **EVERY** power supply should have:
      - Fuse in AC input line.
      - On/off switch in AC input line.
      - Bleeder resistor.
        - High value resistor across output of power supply.
        - Discharges filter capacitors.



# Practical Circuits

- Rectifiers & Power Supplies
  - Switchmode or Switching Power Supplies.
    - AC input voltage is rectified & fed to a solid-state oscillator.
    - Oscillator generates series of high-frequency pulses.
      - 20 kHz or greater.
    - Pulses are applied to the primary of a transformer.
    - Output of secondary is filtered & sent to load.
    - Voltage regulated by varying width of pulses fed to transformer.



# Practical Circuits

- Rectifiers & Power Supplies
  - Switchmode or Switching Power Supplies.
    - High frequency allows use of much smaller transformer.
    - High frequency allows use of much smaller capacitors.
      - Low effective series inductance (ESL).
    - High frequency allows use of much smaller inductors.
    - High frequency allows rapid response to load changes.




# Practical Circuits

- Rectifiers & Power Supplies
  - Switchmode or Switching Power Supplies.
    - Advantages over linear power supplies.
      - Smaller size.
      - Less weight.
      - Higher efficiency.
    - Disadvantages over linear power supplies.
      - RF noise generation.
      - Higher cost.


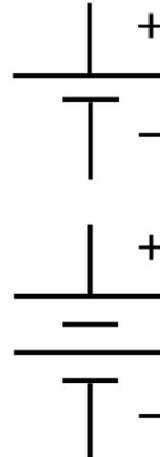
# Practical Circuits

- Batteries & Chargers
  - Batteries.
    - Produce energy by electrochemical reaction.
    - Used by amateurs for:
      - Hand-Held operations.
      - Portable operations.
      - Mobile operations.
      - Emergency operations.



# Practical Circuits

- Batteries & Chargers
  - Batteries.
    - Primary.
      - Electrochemical reaction is not reversible.
      - Battery cannot be recharged.
      - Examples:
        - Carbon-Zinc
        - Alkaline.
        - Silver-Nickel.
        - Lithium.
        - Mercury.
        - Silver-Oxide.





# Practical Circuits

- Batteries & Chargers
  - Batteries.
    - Secondary.
      - Electrochemical reaction is reversible.
      - Battery can be recharged.
      - Examples:
        - Lead-Acid.
        - Nickel-Cadmium (NiCad).
        - Nickel-Metal-Hydrate (NiMH).
        - Lithium-Ion (Li-Ion).



# Practical Circuits

- Batteries & Chargers
  - Batteries.
    - Discharge at low rate.
      - Less internal heating.
      - NiCad & NiMH batteries have low internal resistance & are designed for high discharge currents.
    - All batteries have some leakage.
      - Self-discharge.
        - Store in cool, dry location.
    - 12-volt lead-acid batteries should not be discharged below 10.5 volts.



# Practical Circuits

- Batteries & Chargers
  - Charging Batteries.
    - **NEVER** attempt to recharge a primary-cell battery.
    - **ALWAYS** use proper charger.
      - NiCad & NiMH batteries are charged with constant current until voltage rises to specified value.
      - Lead-Acid batteries are charged with constant voltage until current drops to specified value.
    - **ALWAYS** provide proper ventilation.
      - Lead-Acid batteries give off hydrogen gas during charging. **(Remember the Hindenburg!)**



# Practical Circuits

- Alternative Power
  - Generators
    - Gasoline or Diesel Powered.
    - <1kW to >10kW.






# Practical Circuits

- Alternative Power
  - Solar Power
    - If sufficient light falls on a P-N junction, free electrons in the N-type material will absorb energy & flow across the junction into the P-type material.
      - Most common material is Silicon.
      - Most efficient material is Gallium-Arsenide.
      - Fully-illuminated junction yields about 0.5 VDC.
      - Almost 1 kW/m<sup>2</sup>.
      - Rapidly becoming commercially viable for power generation.



# Practical Circuits

- Alternative Power
  - Solar Power

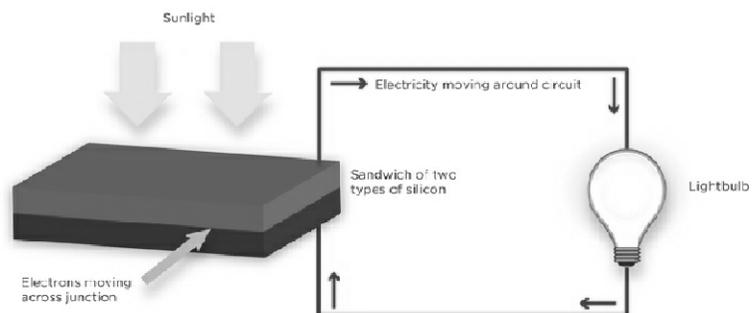



# Practical Circuits

- Alternative Power
  - Wind Power
    - DC generator attached to propeller.



# Practical Circuits

- Alternative Power
  - Energy Storage.
    - Solar power & wind power are not continuously available.
    - Must store energy during periods of daylight or when the wind is blowing to save up for nighttime or when the wind is calm.
      - Storage batteries most commonly used.
      - Solar system have diode in series between solar panel & batteries to prevent discharging batteries back through the panel during low-light conditions.



# Practical Circuits

- Connectors
  - Convenient way to make electrical connections.
  - Terminology.
    - Pins = Contacts that extend out of connector body.
    - Sockets = Hollow, recessed contacts.
    - Connectors with pins are “male”.
    - Connectors with sockets are “female”.




# Practical Circuits

- Connectors
  - Terminology (cont'd).
    - Connectors with specially-shaped bodies or pin/socket arrangements are call “keyed connectors”.
      - Keyed connectors avoid damage caused by mis-mating connectors.
    - Plugs = Connectors installed on ends of cables.
    - Jacks = Connectors installed on equipment.


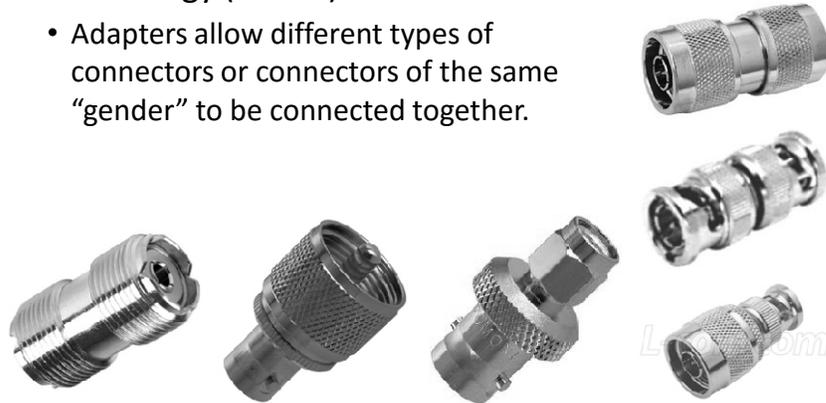
# Practical Circuits

- Connectors
  - Terminology (cont'd).
    - Adapters allow different types of connectors or connectors of the same "gender" to be connected together.



# Practical Circuits

- Connectors
  - Power Connectors.
    - Coaxial Power Connectors.
      - Low current.
      - Commonly used on hand-held transceivers and station accessories.





# Practical Circuits

- Connectors

- Power Connectors.

- Molex® Connectors.

- Many HF transceivers use the 6-pin connector.
      - Pins paralleled to increase current capacity.
      - Many VHF/UHF transceivers use the 2-pin connector.




# Practical Circuits

- Connectors

- Power Connectors.

- Anderson PowerPole® Connectors.

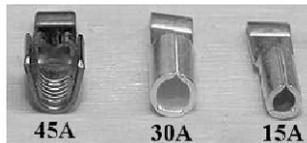- Becoming increasingly popular for station interconnections.
      - Easy to install with proper crimp tool.





# Practical Circuits

- Connectors
  - Power Connectors.
    - Terminal Strips.



# Practical Circuits

- Connectors
  - Audio and Control Connectors.
    - Phone plugs & jacks (TRS connectors).
      - Audio.
      - Keys.
      - Control signals.
      - Sizes:
        - Standard -- 1/4" dia.
        - Aircraft -- 0.206" dia. (Rare)
        - Miniature -- 1/8" (3.5 mm) dia.
        - Sub-miniature -- 3/32" (2.5 mm) dia.






# Practical Circuits

- Connectors
  - Audio and Control Connectors.
    - RCA Phono plugs & jacks.
      - Audio.
      - Low-level RF.
      - Control Signals.


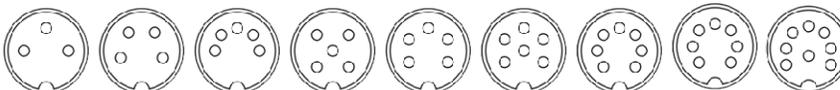
# Practical Circuits


- Connectors
  - Audio and Control Connectors.
    - DIN connectors.
      - *Deutsches Institut für Normung*
        - German national standards organization.
      - Audio.
      - Control Signals.




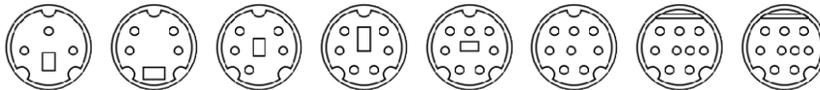
# Practical Circuits

- Connectors
  - Audio and Control Connectors.
    - Mini-DIN connectors.
      - Audio.
      - Control Signals.



# Practical Circuits

- Connectors
  - RF Connectors.
    - UHF.
      - Plug = PL-259.
      - Socket = SO-239.
      - $\leq 150$  MHz.
      - $\geq 1.5$  kW.
      - $\leq 500 V_{\text{Peak}}$
      - Non-constant impedance.
      - Not weather resistant.
      - Inexpensive.





# Practical Circuits

- Connectors
  - RF Connectors.
    - N.
      - $\leq 10$  GHz.
      - $\geq 1.5$  kW.
      - $\leq 1500$  V<sub>Peak</sub>
      - Constant impedance.
        - $50 \Omega$  or  $75 \Omega$  versions available.
      - Weather-resistant.
      - More expensive than UHF connectors.



# Practical Circuits

- Connectors
  - RF Connectors.
    - BNC.
      - $\leq 4$  GHz.
      - Low power.
      - $\leq 500$  V<sub>Peak</sub>
      - Constant impedance.
        - $50 \Omega$  or  $75 \Omega$  versions available.





# Practical Circuits

- Connectors
  - RF Connectors.
    - SMA.
      - $\leq 18$  GHz.
      - Low Power
      - $\leq 250$  V<sub>RMS</sub>
      - Constant impedance.
        - $50 \Omega$ .



# Practical Circuits


- Connectors
  - Data Connectors.
    - D-Subminiature Connectors.
      - DB-25
        - Serial (COM) ports.
        - Parallel printer ports.
      - DE-9
        - Incorrectly known as DB-9.
        - Serial (COM) ports.




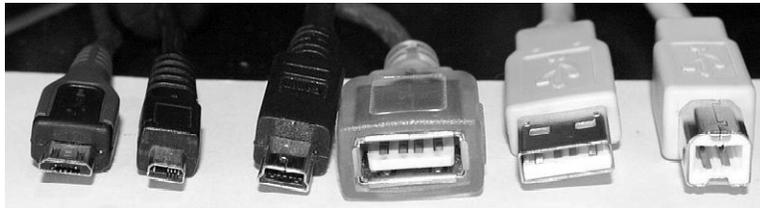
# Practical Circuits

- Connectors
  - Data Connectors.
    - USB Connectors.
      - USB replacing RS-232.
      - Many manufacturers making devices to interconnect transceivers & other station equipment using USB.



**G4E08 -- What is the name of the process by which sunlight is changed directly into electricity?**

- A. Photovoltaic conversion
- B. Photon emission
- C. Photosynthesis
- D. Photon decomposition



**G4E09 -- What is the approximate open-circuit voltage from a fully illuminated silicon photovoltaic cell?**

- A. 0.02 VDC
- B. 0.5 VDC
- C. 0.2 VDC
- D. 1.38 VDC



**G4E10 -- What is the reason that a series diode is connected between a solar panel and a storage battery that is being charged by the panel?**

- A. The diode serves to regulate the charging voltage to prevent overcharge
- B. The diode prevents self discharge of the battery though the panel during times of low or no illumination
- C. The diode limits the current flowing from the panel to a safe value
- D. The diode greatly increases the efficiency during times of high illumination



**G4E11 -- Which of the following is a disadvantage of using wind as the primary source of power for an emergency station?**

- A. The conversion efficiency from mechanical energy to electrical energy is less than 2 percent
- B. The voltage and current ratings of such systems are not compatible with amateur equipment
- ➔ C. A large energy storage system is needed to supply power when the wind is not blowing
- D. All of these choices are correct



**G6A01 -- What is the minimum allowable discharge voltage for maximum life of a standard 12 volt lead acid battery?**

- A. 6 volts
- B. 8.5 volts
- ➔ C. 10.5 volts
- D. 12 volts



**G6A02 -- What is an advantage of the low internal resistance of nickel-cadmium batteries?**

- A. Long life
- ➔ B. High discharge current
- C. High voltage
- D. Rapid recharge



**G6B04 -- When is it acceptable to recharge a carbon-zinc primary cell?**

- A. As long as the voltage has not been allowed to drop below 1.0 volt
- B. When the cell is kept warm during the recharging period
- C. When a constant current charger is used
- ➔ D. Never



**G6B12 -- Which of the following connectors would be a good choice for a serial data port?**

- A. PL-259
- B. Type N
- C. Type SMA
- D. DE-9



**G6B13 -- Which of these connector types is commonly used for RF connections at frequencies up to 150 MHz?**

- A. Octal
- B. RJ-11
- C. PL-259
- D. DB-25



**G6B14 -- Which of these connector types is commonly used for audio signals in Amateur Radio stations?**

- A. PL-259
- B. BNC
- C. RCA Phono
- D. Type N



**G6B15 -- What is the main reason to use keyed connectors instead of non-keyed types?**

- A. Prevention of use by unauthorized persons
- B. Reduced chance of incorrect mating
- C. Higher current carrying capacity
- D. All of these choices are correct



**G6B16 -- Which of the following describes a type-N connector?**

- ➔ A. A moisture-resistant RF connector useful to 10 GHz
- B. A small bayonet connector used for data circuits
- C. A threaded connector used for hydraulic systems
- D. An audio connector used in surround-sound installations



**G6B17 -- What is the general description of a DIN type connector?**

- A. A special connector for microwave interfacing
- B. A DC power connector rated for currents between 30 and 50 amperes
- ➔ C. A family of multiple circuit connectors suitable for audio and control signals
- D. A special watertight connector for use in marine applications



**G6B18 -- What is a type SMA connector?**

- A. A large bayonet-type connector usable at power levels in excess of 1 KW
- ➔ B. A small threaded connector suitable for signals up to several GHz
- C. A connector designed for serial multiple access signals
- D. A type of push-on connector intended for high-voltage applications



**G7A01 -- What safety feature does a power-supply bleeder resistor provide?**

- A. It acts as a fuse for excess voltage
- ➔ B. It ensures that the filter capacitors are discharged when power is removed
- C. It removes shock hazards from the induction coils
- D. It eliminates ground-loop current



**G7A02 -- Which of the following components are used in a power-supply filter network?**

- A. Diodes
- B. Transformers and transducers
- C. Quartz crystals
- D. Capacitors and inductors



**G7A03 -- What is the peak-inverse-voltage across the rectifiers in a full-wave bridge power supply?**

- A. One-quarter the normal output voltage of the power supply
- B. Half the normal output voltage of the power supply
- C. Double the normal peak output voltage of the power supply
- D. Equal to the normal peak output voltage of the power supply



**G7A04 -- What is the peak-inverse-voltage across the rectifier in a half-wave power supply?**

- A. One-half the normal peak output voltage of the power supply
- B. One-half the normal output voltage of the power supply
- C. Equal to the normal output voltage of the power supply
- D. Two times the normal peak output voltage of the power supply



**G7A05 -- What portion of the AC cycle is converted to DC by a half-wave rectifier?**

- A. 90 degrees
- B. 180 degrees
- C. 270 degrees
- D. 360 degrees



**G7A06 -- What portion of the AC cycle is converted to DC by a full-wave rectifier?**

- A. 90 degrees
- B. 180 degrees
- C. 270 degrees
- D. 360 degrees



**G7A07 -- What is the output waveform of an unfiltered full-wave rectifier connected to a resistive load?**

- A. A series of DC pulses at twice the frequency of the AC input
- B. A series of DC pulses at the same frequency as the AC input
- C. A sine wave at half the frequency of the AC input
- D. A steady DC voltage



**G7A08 -- Which of the following is an advantage of a switch-mode power supply as compared to a linear power supply?**

- A. Faster switching time makes higher output voltage possible
- B. Fewer circuit components are required
- C. High frequency operation allows the use of smaller components
- D. All of these choices are correct



## Basic Test Equipment

- Analog & Digital Meters
  - Multimeters.
    - a.k.a. – VOM, DVM, VTVM.
    - Accuracy expressed in % of full scale.
      - If accuracy is 2% of full scale on 100 mA scale, then accuracy is  $\pm 2$  mA.
    - Resolution expressed in digits.
      - Typically  $3\frac{1}{2}$  digits (0.000 to 1.999)
      - $3\frac{1}{2}$  digit  $\rightarrow$  0.05% resolution.
    - **DO NOT CONFUSE RESOLUTION WITH ACCURACY!**





## Basic Test Equipment

- Analog & Digital Meters
  - For most accurate results, meters should have little or no effect on the value being measured.
    - A voltmeter should have the highest input impedance as possible.
    - An ammeter should have the lowest series resistance as possible.



## Basic Test Equipment

- Analog & Digital Meters
  - Multimeters.
    - Analog.
      - D'Arsonval movement.
        - Rotating coil suspended between permanent magnets.
        - When current flows in coil, coil rotates moving needle across scale.
        - Coil impedance affects accuracy.
    - Sensitivity expressed in Ohms/Volt.
      - 20,000  $\Omega/V$  = very good analog voltmeter.





# Basic Test Equipment

- Analog & Digital Meters
  - Multimeters
    - Vacuum Tube Voltmeters.
      - D'Arsonval movement.
      - Used vacuum tube amplifier to improve sensitivity.
        - Typically 10 meg $\Omega$ /V or greater.



# Basic Test Equipment

- Analog & Digital Meters
  - Multimeters
    - Digital Meters.
      - Uses high input impedance FET amplifier to improve sensitivity.
        - Typically 10 M $\Omega$ /V or greater.
      - Uses internal microprocessor to perform measurement calculations.







## Basic Test Equipment

- Analog & Digital Meters
  - Analog Meters.
    - Faster response times
    - Easier to use when adjusting a circuit.
      - e.g., Tuning an amplifier.
  - Digital Meters.
    - Higher sensitivity.
    - Higher resolution.


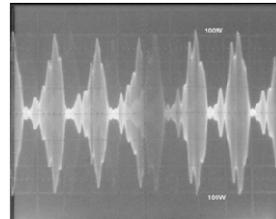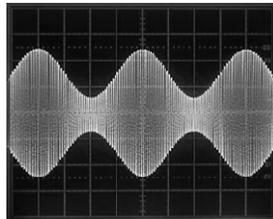
## Basic Test Equipment

- The Oscilloscope
  - Real-time display of rapidly-changing audio or RF signals.
    - Keying waveform of CW signal.
  - Voltage measurements of complex waveforms.





## Basic Test Equipment

- The Oscilloscope
  - Displays voltage versus time.
    - Signal applied to vertical deflection plates.
    - Sawtooth waveform from a time base applied to horizontal deflection plates.
  - Bandwidth of vertical amplifier determines highest frequency signal that can be displayed.
  - Sometimes 2 or more vertical amplifiers.
    - Allows displaying multiple signals simultaneously.



## Basic Test Equipment

- Signal Generators
  - Generate accurate signals.
    - Precise amplitude.
    - Different waveforms.
      - Sine wave.
      - Square wave.
      - Sawtooth wave.
      - Pulse train.





## Basic Test Equipment

- Signal Generators
  - Service Monitors
    - Equipment designed for testing communications equipment.
      - Signal generator.
        - Precise voltage.
        - Precise frequency.
        - AM modulation.
        - FM modulation.
      - Frequency counter.
      - Power meter.
      - Dummy load.



## Basic Test Equipment


- Impedance & Resonance Measurements
  - Antenna Analyzer.
    - Impedance.
      - Resistance.
      - Reactance.
    - Standing-wave-ratio (SWR).
    - Cable velocity factor.
    - Cable electrical length.
    - Distance to fault.
    - Susceptible to interference from strong nearby transmitters.




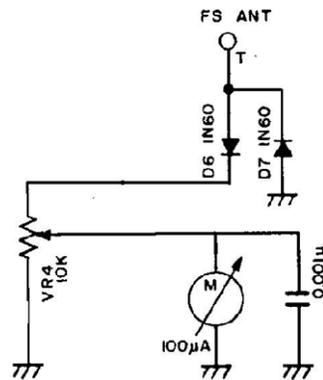
## Basic Test Equipment

- Field Strength & RF Power Meters
  - Field Strength Meters.
    - Measures relative strength of RF field.
    - Determine antenna pattern.
    - Close-in direction finding.



## Basic Test Equipment

- Field Strength & RF Power Meters
  - RF Power Meters.
    - Directional Wattmeter.
      - Measure forward power.
      - Measure reflected power.
      - Calculate SWR.





**G4B01 -- What item of test equipment contains horizontal and vertical channel amplifiers?**

- A. An ohmmeter
- B. A signal generator
- C. An ammeter
- D. An oscilloscope



**G4B02 -- Which of the following is an advantage of an oscilloscope versus a digital voltmeter?**

- A. An oscilloscope uses less power
- B. Complex impedances can be easily measured
- C. Input impedance is much lower
- D. Complex waveforms can be measured



**G4B03 -- Which of the following is the best instrument to use when checking the keying waveform of a CW transmitter?**

- A. An oscilloscope
- B. A field-strength meter
- C. A sidetone monitor
- D. A wavemeter



**G4B04 -- What signal source is connected to the vertical input of an oscilloscope when checking the RF envelope pattern of a transmitted signal?**

- A. The local oscillator of the transmitter
- B. An external RF oscillator
- C. The transmitter balanced mixer output
- D. The attenuated RF output of the transmitter



**G4B05 -- Why is high input impedance desirable for a voltmeter?**

- A. It improves the frequency response
- B. It decreases battery consumption in the meter
- C. It improves the resolution of the readings
- ➔ D. It decreases the loading on circuits being measured



**G4B06 -- What is an advantage of a digital voltmeter as compared to an analog voltmeter?**

- A. Better for measuring computer circuits
- B. Better for RF measurements
- ➔ C. Better precision for most uses
- D. Faster response



**G4B08 -- Which of the following instruments may be used to monitor relative RF output when making antenna and transmitter adjustments?**

- A. A field-strength meter
- B. An antenna noise bridge
- C. A multimeter
- D. A Q meter



**G4B09 -- Which of the following can be determined with a field strength meter?**

- A. The radiation resistance of an antenna
- B. The radiation pattern of an antenna
- C. The presence and amount of phase distortion of a transmitter
- D. The presence and amount of amplitude distortion of a transmitter



**G4B10 -- Which of the following can be determined with a directional wattmeter?**

- A. Standing wave ratio
- B. Antenna front-to-back ratio
- C. RF interference
- D. Radio wave propagation



**G4B11 -- Which of the following must be connected to an antenna analyzer when it is being used for SWR measurements?**

- A. Receiver
- B. Transmitter
- C. Antenna and feed line
- D. All of these choices are correct



**G4B12 -- What problem can occur when making measurements on an antenna system with an antenna analyzer?**

- A. Permanent damage to the analyzer may occur if it is operated into a high SWR
- ➔ B. Strong signals from nearby transmitters can affect the accuracy of measurements
- C. The analyzer can be damaged if measurements outside the ham bands are attempted
- D. Connecting the analyzer to an antenna can cause it to absorb harmonics



**G4B13 -- What is a use for an antenna analyzer other than measuring the SWR of an antenna system?**

- A. Measuring the front to back ratio of an antenna
- B. Measuring the turns ratio of a power transformer
- ➔ C. Determining the impedance of an unknown or unmarked coaxial cable
- D. Determining the gain of a directional antenna



**G4B14 -- What is an instance in which the use of an instrument with analog readout may be preferred over an instrument with a numerical digital readout?**

- A. When testing logic circuits
- B. When high precision is desired
- C. When measuring the frequency of an oscillator

→ D. When adjusting tuned circuits



# Questions?





# Next Week

## Chapter 5

# Radio Signals & Equipment